

# Analog Electronic Circuits (EC2.103) : Course project

Spring 2024, IIIT Hyderabad, Due date : 7<sup>th</sup> May, 2024 (18:00 hrs)

Instructor: Prof. Abhishek Srivastava, CVEST, IIIT Hyderabad

## Instructions:

1. Key dates: 20<sup>th</sup> April (Saturday), 7<sup>th</sup> May (Tuesday), 8<sup>th</sup> May (Wednesday)
2. Max 2 students per group
3. Submit your project report in [two column format](#) as a single pdf (Name\_group\_number.pdf) on moodle by the due date. [Only latex/word/notion](#) submissions are allowed
4. Report should be self explanatory and must carry complete solution - Answers with schematics, SPICE directives, annotated waveforms, inference/discussion on results
5. [Intermediate evaluation \(40% weight\)](#) will be held on 20<sup>th</sup> April (Saturday) during the lab hours. Prepare a [brief presentation](#) (few slides) showing complete circuit diagrams, calculations, component values, simulation results. Be ready to run LTSpice simulations for all modules and demonstrate working of few hardware modules
6. Clearly highlight the [contributions](#) of each group member during the presentation
7. Final presentation/demonstration and viva will be held on 8<sup>th</sup> May (Wed)
8. Use the given model files TSMC\_180nm.txt (NMOS/PMOS) and UA741.301(opamp) for simulations
9. Specify MOSFET parameters W, L, AS, AD, PS, PD for all simulations

## Quadrature down converter

Fig. 1 depicts a quadrature down converter (QDC) that is commonly used in modern day wireless receivers (RX) such as Bluetooth, Wi-Fi and WLAN. Quadrature downconversion helps in interference mitigation and improves the quality of communication. In this project, we will implement a prototype of QDC for given specifications.

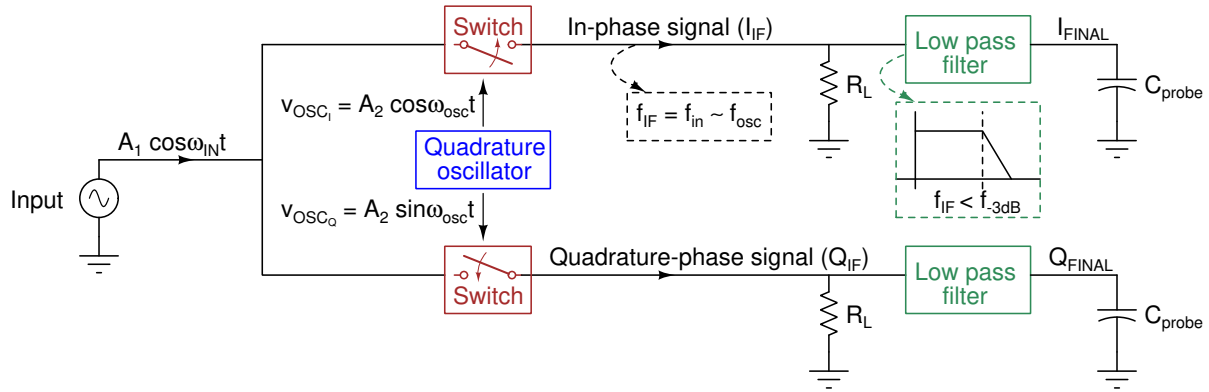


Figure 1

As shown in Fig. 1, the input signal  $v_{in} = A_1 \cos \omega_{in} t$  is mixed with  $v_{OSC_I} = A_2 \cos \omega_{OSC} t$  and  $v_{OSC_Q} = A_2 \sin \omega_{OSC} t$  to produce in-phase ( $v_{IF_I}$ ) and quadrature-phase ( $v_{IF_Q}$ ) intermediate frequency (IF) signals, respectively. The in-phase and quadrature-phase signals have a phase difference of 90°. Mixing of two signals is equivalent to their multiplication as shown below.

$$v_{IF_I} = v_{in} \times v_{OSC_I} = \frac{A_1 A_2}{2} (\cos(\omega_{in} t - \omega_{OSC} t) + \cos(\omega_{in} t + \omega_{OSC} t))$$

$$v_{IF_Q} = v_{in} \times v_{OSC_Q} = \frac{A_1 A_2}{2} (\sin(\omega_{in} t + \omega_{OSC} t) - \sin(\omega_{in} t - \omega_{OSC} t))$$

As shown in Fig. 1, the mixed signal is fed a low pass filter to pass only the IF signals with frequency  $\omega_{IF} = (\omega_{IN} - \omega_{OSC})$ , which can be sufficiently low value for sufficiently high values of  $\omega_{IN}$  and  $\omega_{osc}$ . For example, if  $f_{IN} = 2.4$  GHz and  $f_{osc} = 2.401$  GHz, then  $f_{IF} = 1$  MHz.

### 1. BONUS QUESTION (not mandatory to submit)

Briefly explain the utility/need of quadrature (I-Q) operation (downconversion/mixing) in modern day wireless receivers. Support your answer with clear diagrams, spectrum depictions and mathematical expressions.

(Suggested references: [1] A. Abidi, 'Direct-Conversion Radio Transceivers for Digital Communications' *IEEE JOURNAL OF SOLID-STATE CIRCUITS*, VOL. 30, NO. 12, DECEMBER 1995. [2] Chapter 3 and 4 from 'RF Microelectronics' (2<sup>nd</sup> edition) by Behzad Razavi. )

### 2. Quadrature oscillator design

Using opamps, design a quadrature oscillator which produces two sinusoidal signals ( $v_{OSC_I}$  &  $v_{OSC_Q}$ ) at 100 kHz with a phase difference of 90° and oscillation amplitude of 1  $V_{p-p}$ .

- Clearly show the topology, calculations for finding component (VDD/VSS/R/C/L/W/L (as applicable)) values and schematic with annotated component values.
- Use the given model file for the opamp for LTSpice simulations. Give plots for  $v_{OSC_I}$  &  $v_{OSC_Q}$  from transient simulation and FFT. Clearly mark the phase difference between two signals on transient plots.
- Realize the circuit in lab by using 741 opamp IC and other passive components. From the measurements, report the transient waveforms and FFT spectrum for the two signals. Please note that you might have to tweak some parameters in actual experiment as compared to the simulation set up.

(Suggested references: [1] Chapter 2 and 14 from 'Microelectronic Circuits' (7<sup>th</sup> edition) by Sedra and Smith. [2] Ron Mancini, "Design of op amp sine wave oscillators", Texas Instrument, 2000. [3] Ralph Holzel, "A Simple Wide-Band Sine Wave Quadrature Oscillator", *IEEE TRANSACTIONS ON INSTRUMENTATION AND MEASUREMENT*, VOL. 42, NO. 3, JUNE 1993.)

### 3. Switch (mixer) design

As shown in Fig. 2, a simple MOSFET can be used as a switch (mixer), where the oscillator signal is applied to the gate of the device, input is applied at the source and the intermediate frequency output is taken at the drain end.

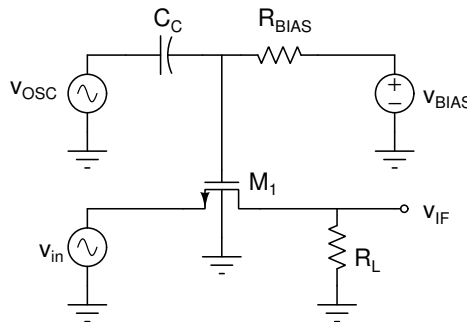


Figure 2

- As shown in Fig. 2, implement the mixer using an NMOS in LTSpice. Clearly mention the values of  $R_{BIAS}$ ,  $C_C$ . Consider  $R_L = 1\text{ k}\Omega$ , amplitude of  $v_{in}$  is 100 mV and frequency is  $f_{IN}$ . Show transient plots of  $v_{in}$ ,  $v_{IF}$  for  $f_{IN} = \{95, 98\text{ kHz}, 99\text{ kHz}, 101\text{ kHz}, 102, 105\text{ kHz}\}$ . Also show corresponding FFT plots for  $v_{IF}$ .
- Realize the circuit in lab using the NMOS transistors and report above component values and plots from measurements. Please note that the NMOS in lab might differ from the one which you use in simulations. For giving  $v_{in}$  and  $v_{osc}$  to the mixer, you can use two function generators in the lab.

#### 4. Low pass filter design

- Design a low pass RC filter (LPF) with -3 dB cut off frequency of 2 kHz. Show the component values with calculations.
- Report frequency response (output magnitude vs frequency) from AC analysis in LTSpice simulations.
- Report transient response for 1 kHz signal and 10 kHz using LTSpice simulations.
- Realize the circuit in lab and report AC and transient plots from measurements.
- Connect mixer setup in previous part and LPF and report results from simulations and measurements.

#### 5. Complete circuit prototype design

Connect all building blocks (oscillator, mixer, filter) and make the complete circuit shown in Fig. 1. Clearly show and tabulate all component/supply values in the schematic.

- Run transient simulations and clearly show waveforms (input, oscillator, IF, IF (FINAL)). Clearly annotate to show the phase difference between the I-Q components.
- Report FFT plots of IF (FINAL- I and Q both). Can you process the FFT plots to find the phase of final I and Q components?
- Realize the complete circuit in lab and report transient plots of  $v_{IN}$ ,  $v_{OSC_I}$ ,  $v_{OSC_Q}$ ,  $v_{IF_I}$ ,  $v_{IF_Q}$ ,  $v_{IF_{FINAL_I}}$  and  $v_{IF_{FINAL_Q}}$  from measurements. Clearly show the corresponding phase difference in the I-Q plots for every result.
- Report FFT plots of  $v_{IF_{FINAL_I}}$  and  $v_{IF_{FINAL_Q}}$  from measurements.
- Make a comparison table for simulation and measurement results showing frequencies (I/Q), phase difference (I/Q), amplitude (I/Q), supply-voltages, bias-voltages, etc. at each relevant node. Also compare the component values used in simulation and measurements.

**Table 1:** Performance summary and comparison

Parameters	Simulated	Measured
Oscillator Frequency		
Oscillator Amplitude (I-phase)		
Oscillator Amplitude (Q-phase)		
Input frequency		
IF		
Supply		
$V_{BIAS}$		
$C_C$		
—		
—		
—		

#### 6. Project report

Make a comprehensive project report in IEEE two column format (shared along with the project problem). **Best design and best report will be awarded.**

#### Other references:

[1] Latex template can be found at following link

<https://www.overleaf.com/latex/templates/ieee-conference-template/grfzhncsfqn>

[2] Lecture notes, tutorials and labs conducted in this course